

# **A Simple 8-bit CPU Implementation on FPGA**

# Motivation


- How CPU execute instruction?
- What is micro-instruction?
- Learn FPGA

# References

- <https://www.youtube.com/user/eaterbc>
- Alto: A personal computer (1979 Xerox)
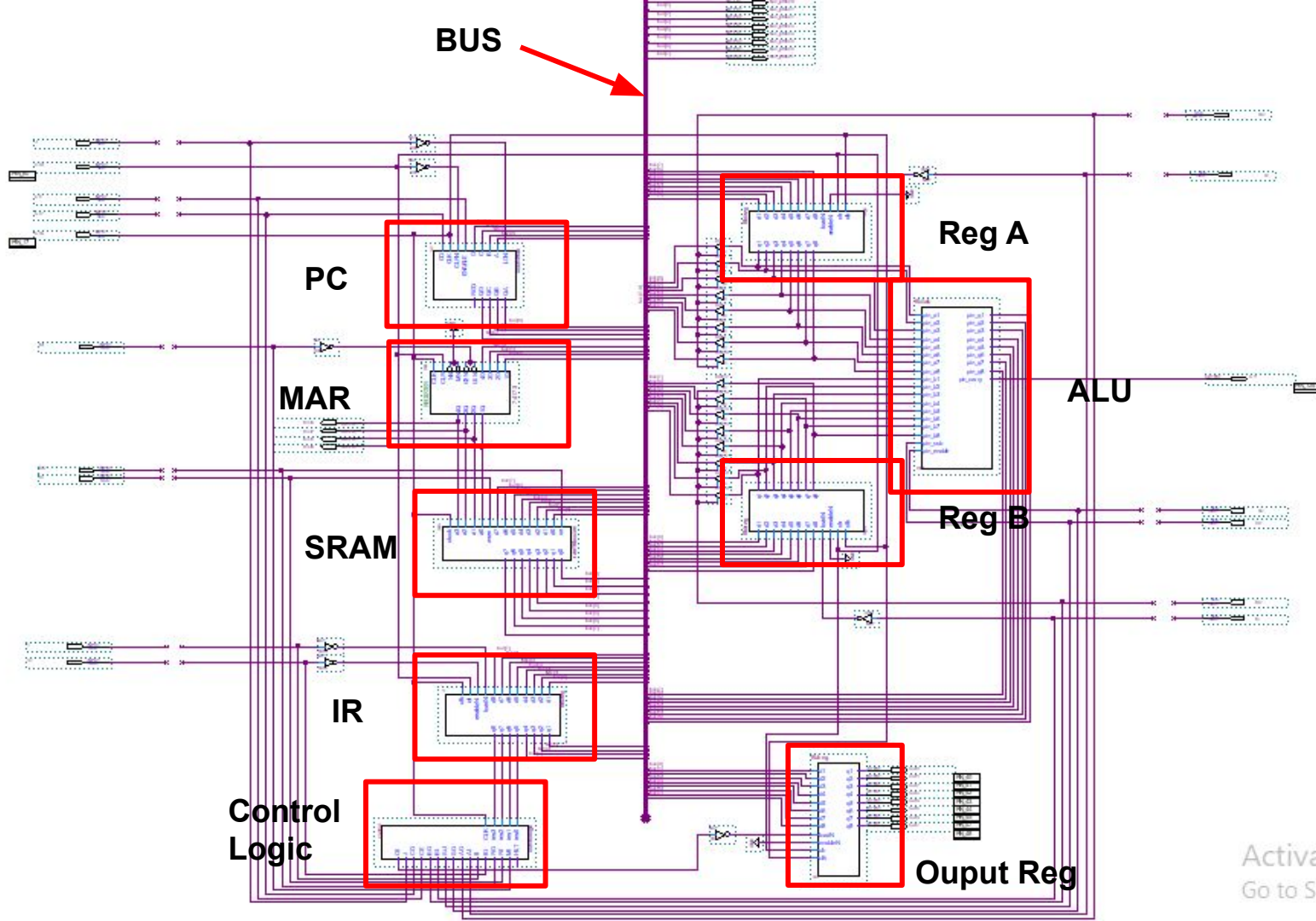
# Overall

- 8-bit instruction length
- 2 general registers
- 4 instructions: LDA, ADD, OUT, HLT
- 16 bytes memory space



# Bus


- Instruction length: 8 bits
  - [4 bits opcode][4 bits mem operand]
- 8-bits bus transfer both address and data
  - 4 bits address
  - 8 bits data

# Register

- MAR: Memory Address Register (4 bits)
- IR: Instruction Register (8 bits)
- General Register A (8 bits)
- General Register B (8 bits)

 
# Memory Address Register

- 74173: 4-bit D-type Register (with 3-state Outputs)
- Control Signals
  - MI (MAR IN)






# 8-bit Register

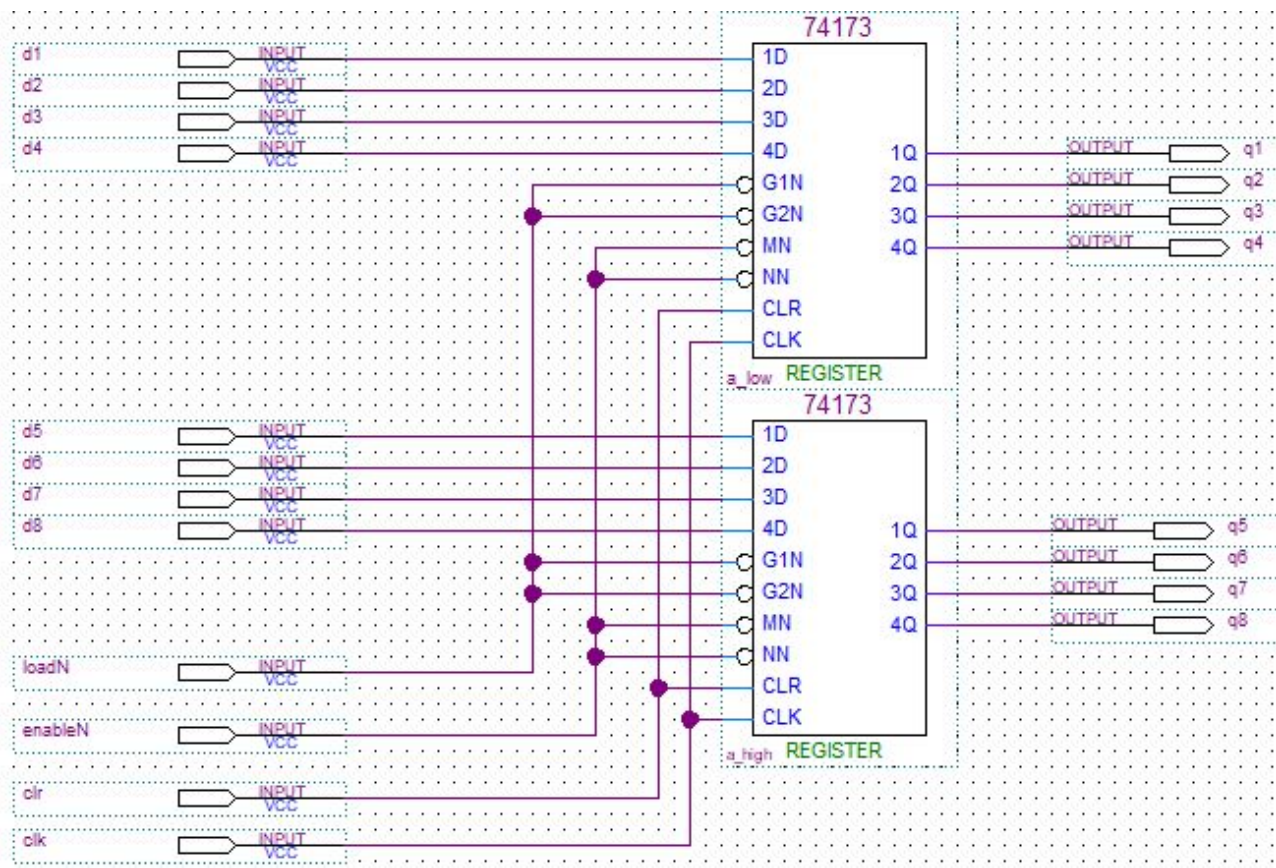


# Instruction Register

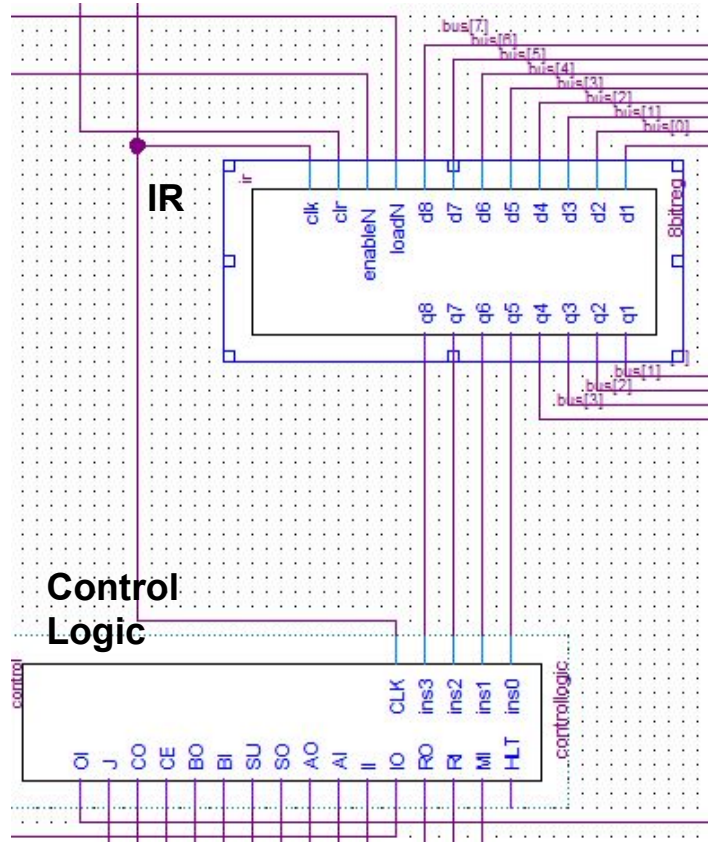

- Input from bus
- Output
  - High 4 bits to control logic
  - Low 4 bits to bus
- Control Signals
  - II (IR IN)
  - IO (IR OUT)

# General Register

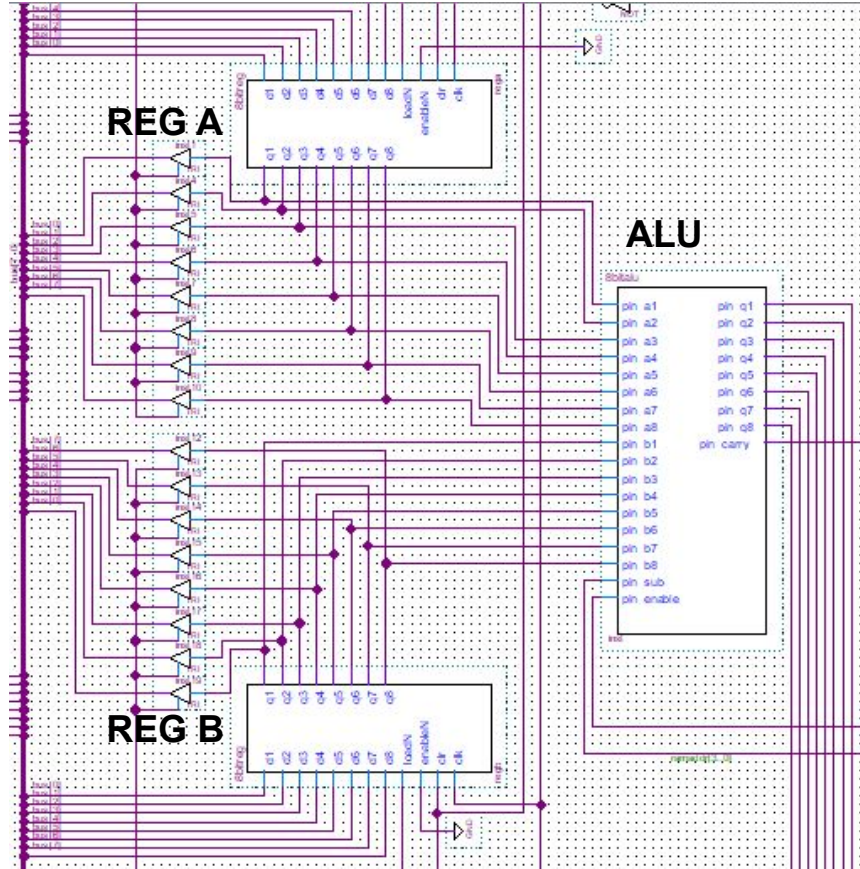



- Input from bus
- Output to both ALU and bus
- Control Signals
  - AI (A IN)
  - AO (A OUT)
  - BI (B IN)
  - BO (B OUT)

# Clock Signal



- Square Wave
- This CPU works on rising edge
- Use Cyclone 2 FPGA's internal clock signal (pin17)

# 4-bit Counter

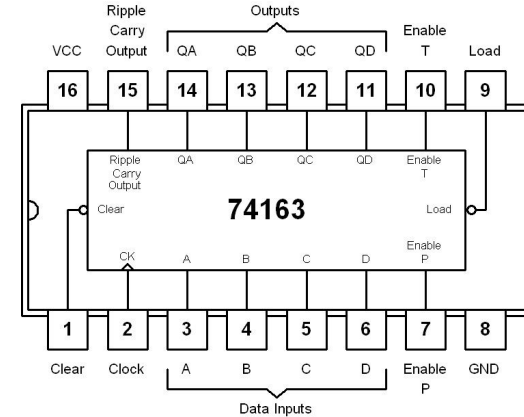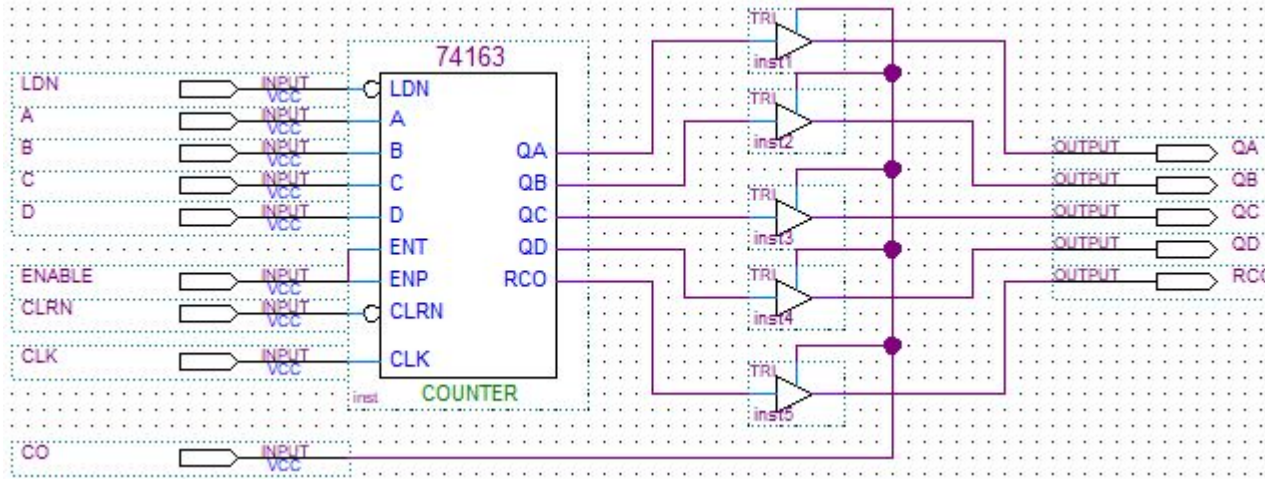


- Control Signals
  - CE (COUNTER ENABLE)
  - CO (COUNTER OUT)

# Memory

- SRAM
- No cache
- Same speed with CPU (1 clock cycle)
- Memory size: 16 byte (4 bits address)




# Memory (cont'd)

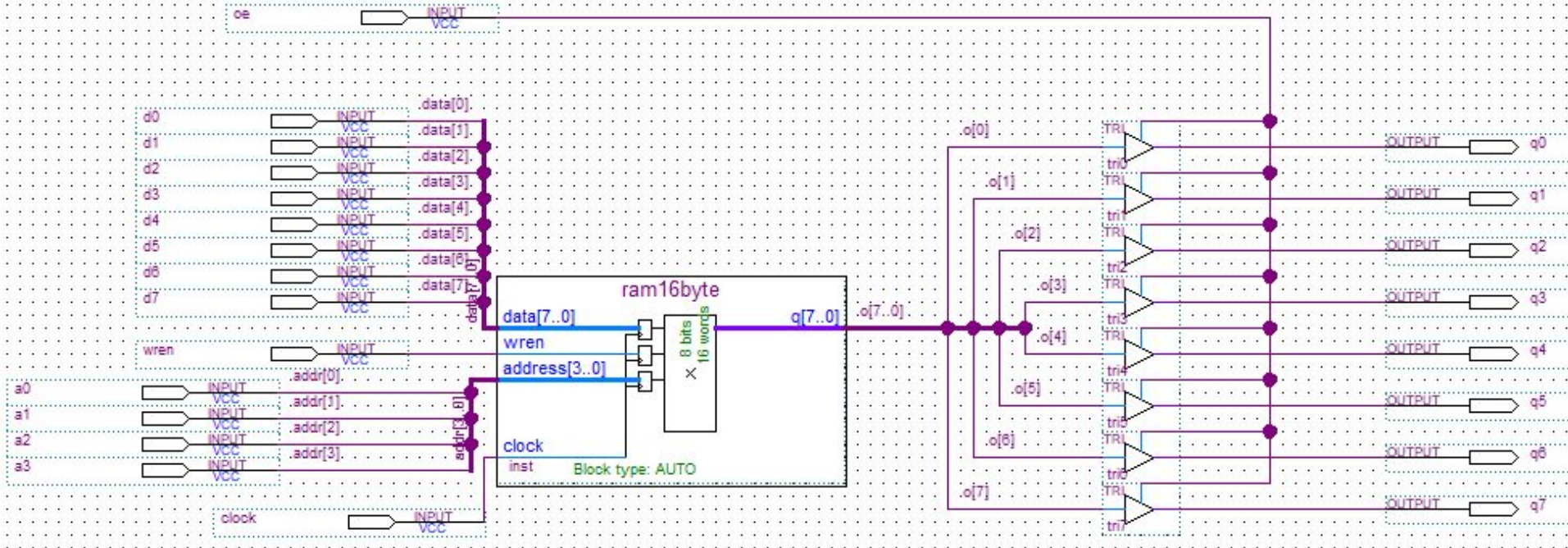

- Quartus ram module

# Memory (cont'd)

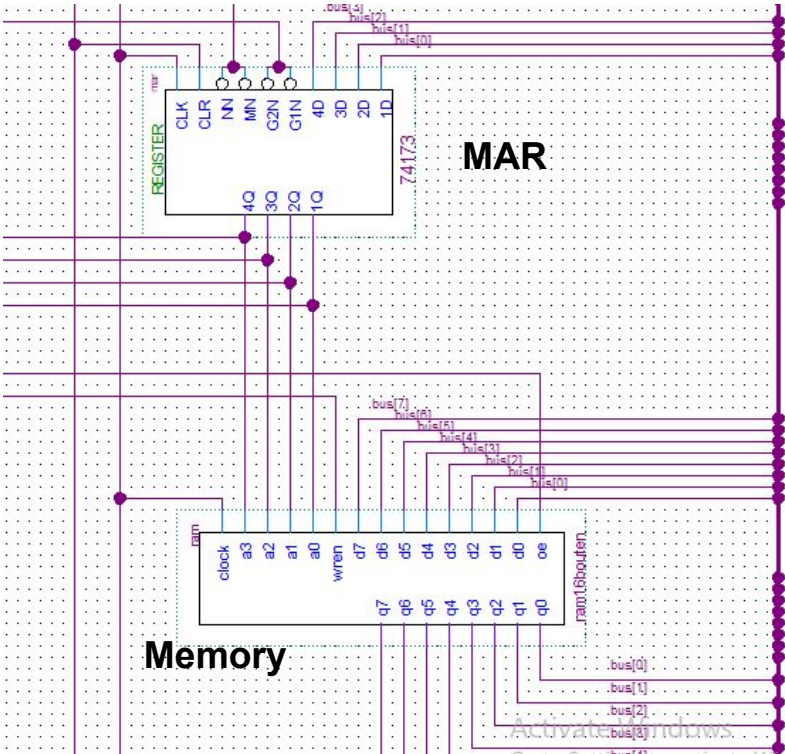

- Input: address from MAR and data from bus
- Output to bus
- Control Signals
  - RI (RAM IN)
  - RO (RAM OUT)

Use mif to set memory data



# Control Logic

- Control Signals
  - HLT MI RI RO IO II AI AO SO SUB BI BO CE CO J OI
- How to use control signals to compose an instruction?
- Example:
  - LDA mem: Load memory into register A
  - LDA 0xE
  - Opcode 0x1 Memory Address 0xE
  - 0001 1110 (0x1E)

# Instruction LDA

LDA instruction takes 4 clock cycle to finish

- |             |   |                                |
|-------------|---|--------------------------------|
| 1. CO MI    | } | <b>Instruction Fetch</b>       |
| 2. RO II CE |   |                                |
| 3. IO MI    |   | <b>Decode</b>                  |
| 4. RO AI    |   | <b>Execute &amp; Writeback</b> |

# Instruction LDA


- Initial state:
  - PC = 0x0000
  - Memory

0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
1E	0	0	0	0	0	0	0	0	0	0	0	0	0	0A	0

↖  
LDA 0xE

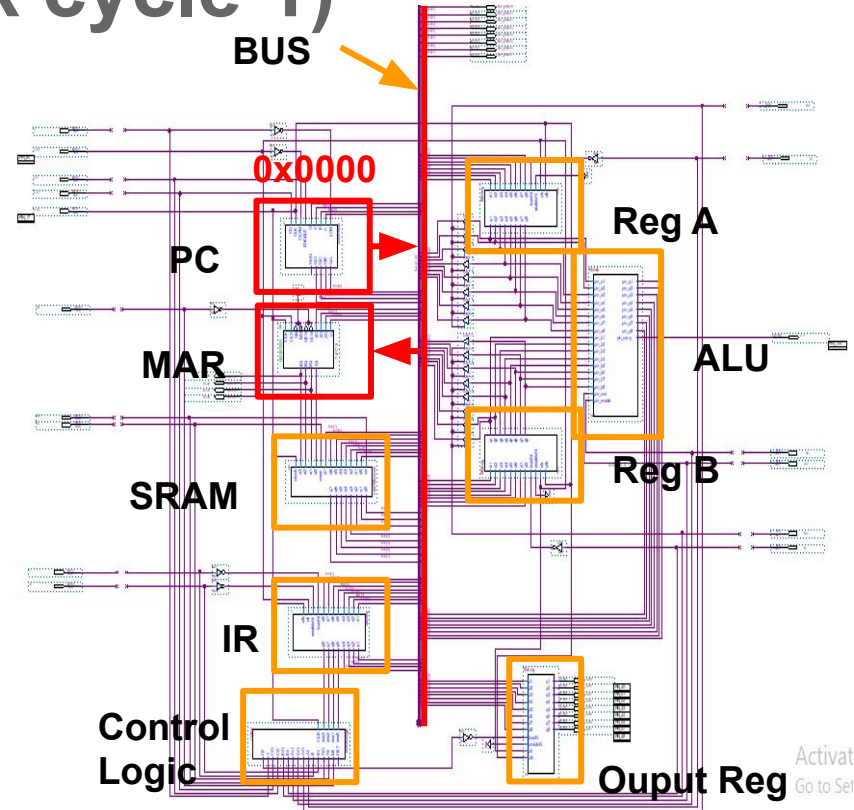
# Fetch instruction (Clock cycle 1)

- CO (COUNTER OUT)  
MI (MAR IN)
- PC  $\rightarrow$  MAR
- Result:
  - MAR = **0x0000**



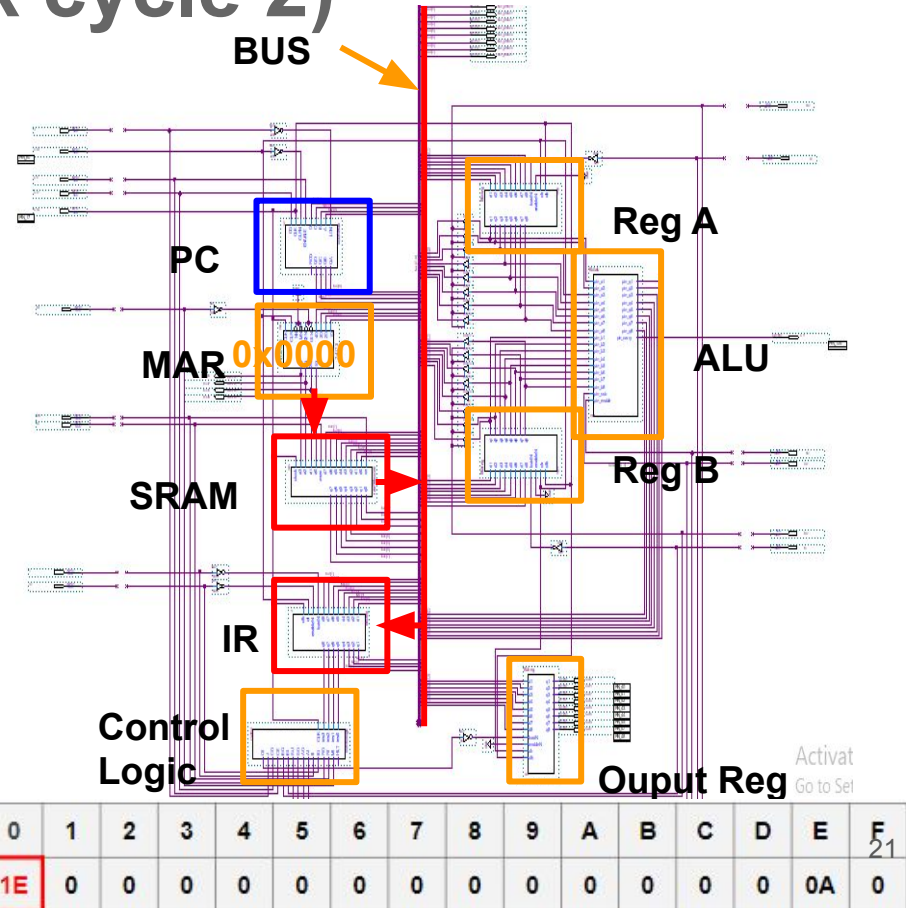
# Fetch instruction (Clock cycle 2)

- RO (RAM OUT)  
II (IR IN)  
CE (COUNTER ENABLE)
- [0x0000] ---> IR  
 $PC = PC + 1$
- Result:
  - IR = **0x1E**
  - PC = **0x1**


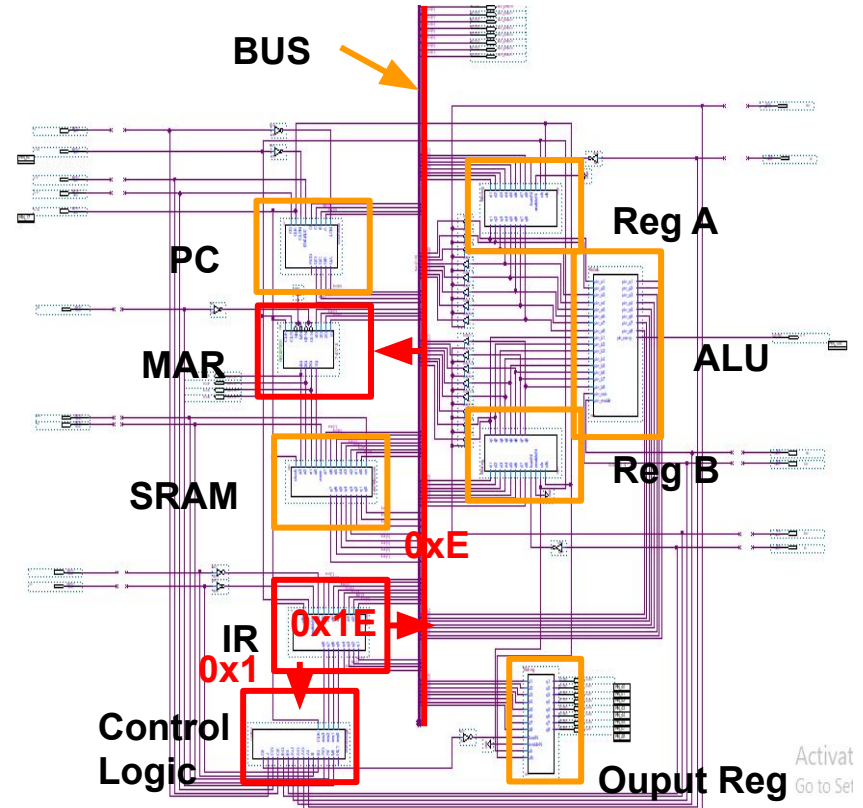
# Decode (Clock cycle 3)

- IO (IR OUT)  
MI (MAR IN)
- IR[0..3] ---> MAR
- Result:
  - MAR = **0xE**




# Execute & Writeback (Clock cycle 4)


- RO (RAM OUT)  
AI (A IN)
- [0xE] ---> RegA

0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
1E	0	0	0	0	0	0	0	0	0	0	0	0	0	0A	0

- Result:
  - RegA = **0x0A**

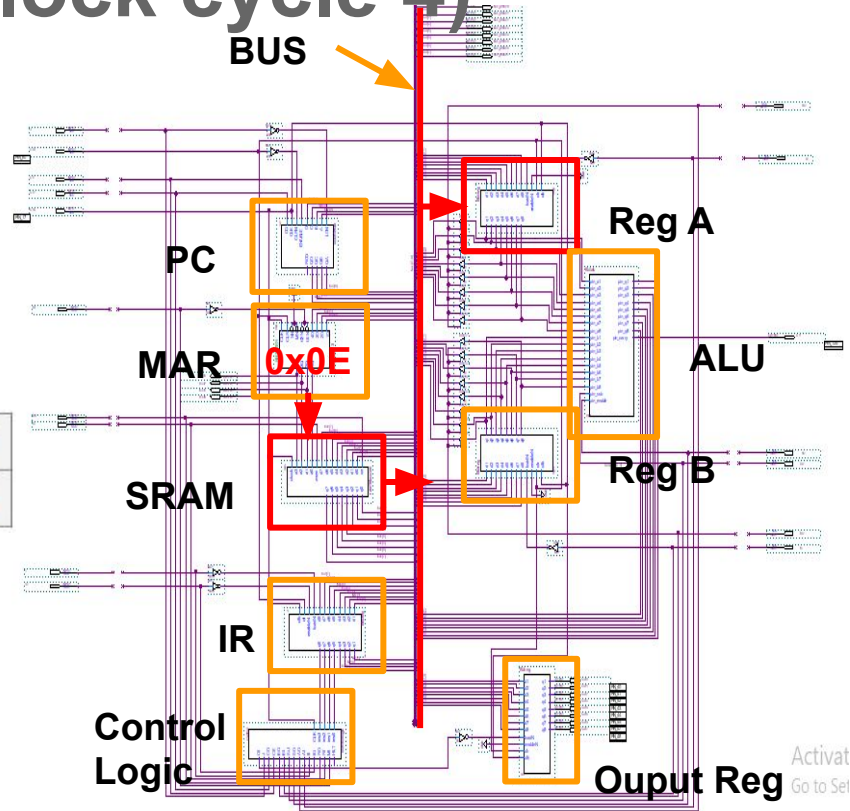

# Control Logic (cont'd)

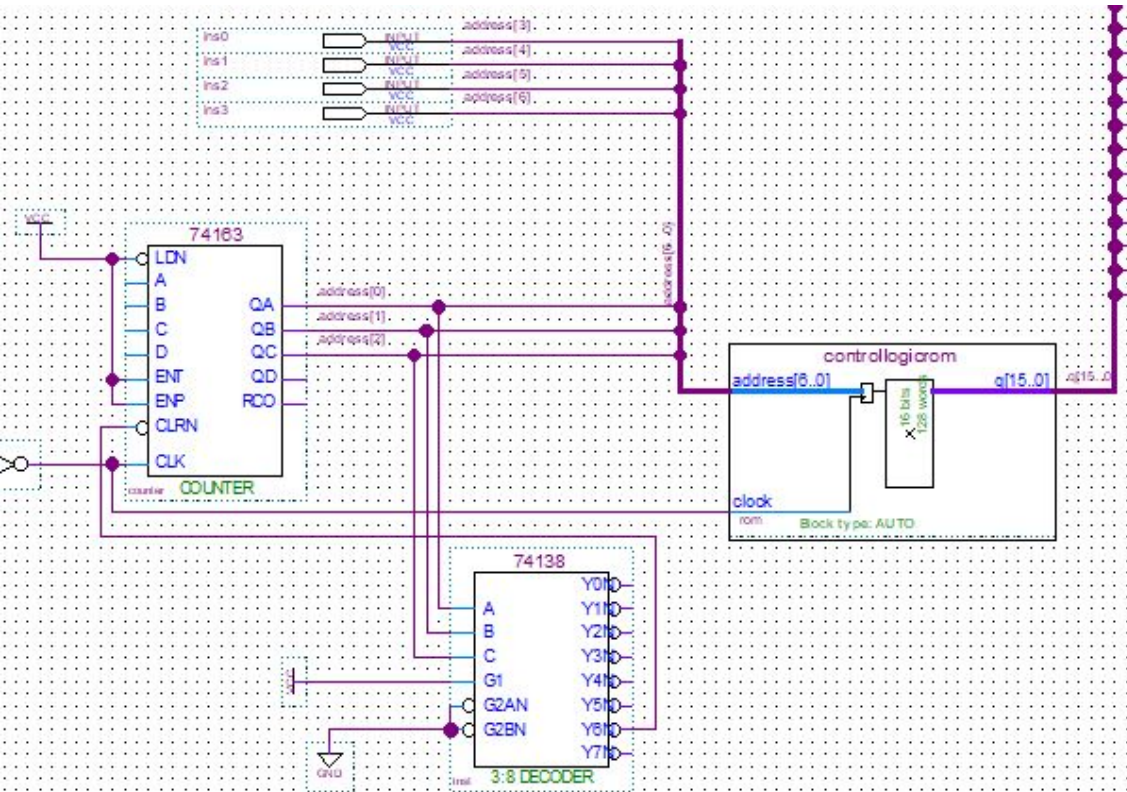


- 4 bits opcode as input
- 6 steps for every instruction
- ROM stores signals for each stage

```
% LDA %
08      : 004004;
09      : 001000;
0A      : 001408;

0B      : 004800;
0C      : 001000;
0D      : 001200;
0E      : 000000;
```




# FPGA

 


- Cyclone II EP2C5 Mini Dev Board

# Display (8 LED lights)


 


# Display (1602A LCD)

 
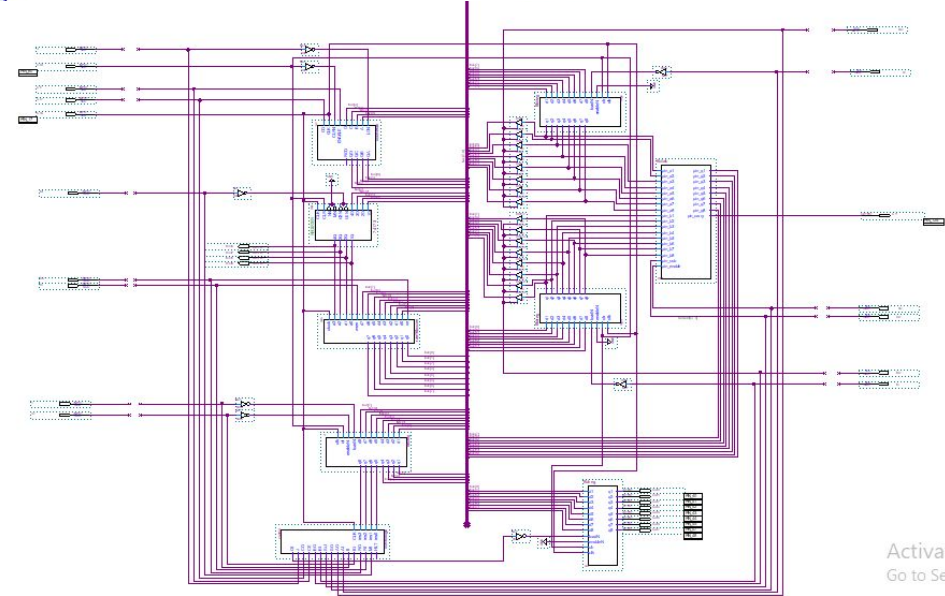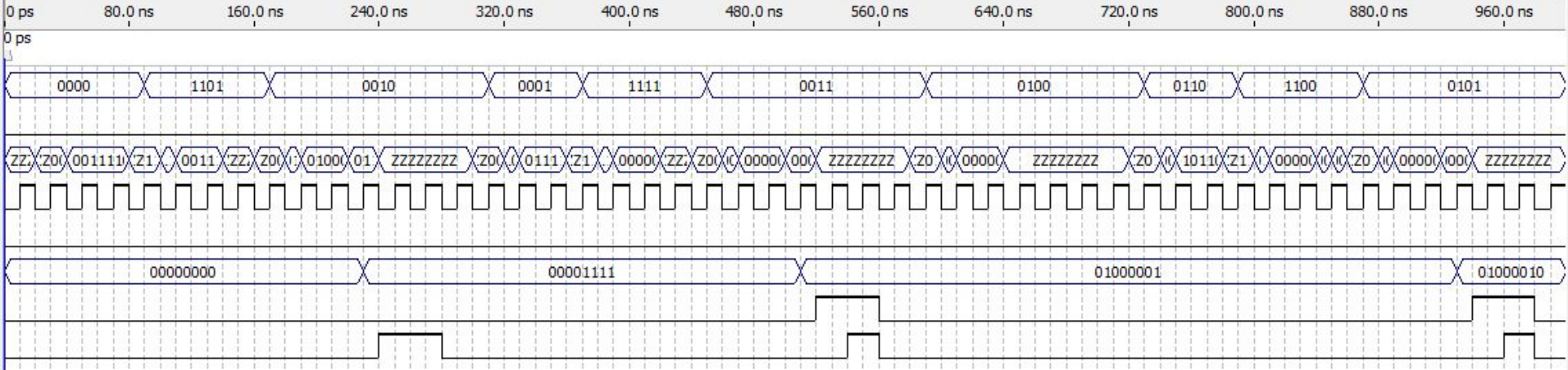
```
00      : 1E;   %LDA 0xe%
01      : 50;   %DISPLAY_CFG%
02      : 1F;   %LDA 0xf%
03      : 40;   %OUT%
04      : 00;   %NOP%
05      : 2C;   %ADD 0xc%
06      : 40;   %OUT%
07      : 00;   %NOP%
08      : 2C;   %ADD 0xc%
09      : 40;   %OUT%
0A      : 30;   %HLT%
0B      : F0;
0C      : 01;
0D      : F0;
0E      : 0F;
0F      : 41;
```





# Thank you!

## Q>